

# Winter\_25\_Quiz\_4 - Results



## Attempt 1 of 1

Written Feb 4, 2025 7:30 PM - Feb 4, 2025 7:45 PM

Attempt Score	16 / 20 - 80 %
Overall Grade (Highest Attempt)	16 / 20 - 80 %

### Question 1

In a multiplexer with 64 data inputs, the number of control inputs is equal to:

- ☐ 4
- ☐ 8
- ☒ 6

### Question 2

What type of digital logic gates are commonly used in the implementation of a digital comparator?

- ☒ XOR gates
- ☐ AND gates
- ☐ NAND gates
- ☐ NOR gates

### Question 3

Using the 8-bit ALU configuration given bellow obtain the Output value?


Using the 8-bit ALU configuration given bellow obtain the Output value?

	A	B	INVA	F0	F1	ENA	ENB	INC	Output
1	00000010	00000111	1	1	1	1	1	1	

- ☐ 00001001  
☒ 00000101  
☐ 00001010  
☐ 11111011
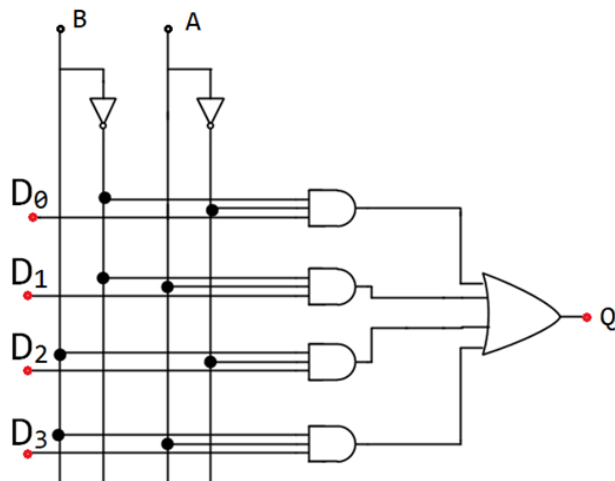
#### Question 4

In the following decoder if A = 1 and B = 0 then the value of Q = ?



- ☐ D3  
☐ D2  
☒ D1  
☐ D0

#### Question 5

If a 8-bit register (R) contains the binary value 0010 0110 (38 in decimal), what is the result of the expression  $R \gg 2$ ?

- ☒ 9.5

- ☐ 9
- ☐ 152
- ☐ 17.5
- ☐ 76

### Question 6

In a multiplexer, what is the purpose of the control inputs?

- ☐ To control the output signal
- ✓ ☒ To select which input to pass to the output
- ☐ To determine the number of inputs
- ☐ To enable or disable the multiplexer

### Question 7

Using the 8-bit ALU configuration given bellow obtain the Output value?

	A	B	INVA	F0	F1	ENA	ENB	INC	Res
1	00000011	00000111	1	0	0	1	1	0	

- ☐ 11111011
- ☐ 00000100
- ☐ 00000111
- ✗ ☐ 00000011

### Question 8

What is the purpose of the carry input (Cin) in a full adder?

- ☐ It represents the carry out from the current adder
- ☐ It represents the borrow in a subtraction operation
- ☐ It represents the borrow out in a subtraction operation
- ✓ ☒ It represents the carry from the previous adder


### Question 9

Which component of an ALU is responsible for performing arithmetic operations?

- ☐ Half adder
- ☐ Decoder
- ☐ Comparator
- ✓ ☒ Full adder

### Question 10

The Q value is :

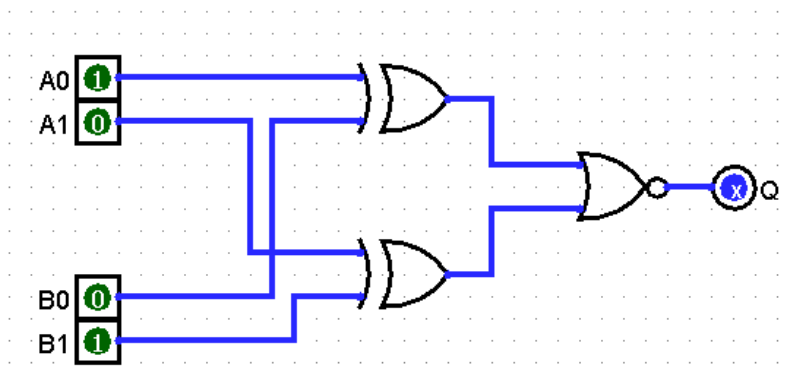

- ☐ none of the mentioned
- ☐ 1
- ✓ ☒ 0

Done