



No E-Mail submissions will be accepted.

Submission formats and file naming:


File name : Pts\_firstName\_lastName\_lab\_3

File format: pdf or MS Word format

e.g. Pts\_Donald\_Trump\_lab\_3.pdf
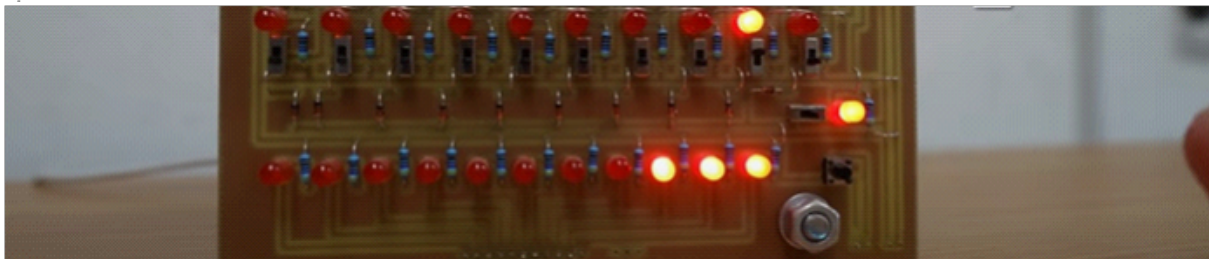
## Reading materials

Use the following link and write a one page summary about the movie.



1) Use truth table to prove the following identities:

(a)  $A + BC = (A+B)(A+C)$

(b)  $A(B+C) = AB + AC$


A	B	C	A+B	A+C	$(A+B)(A+C)$	BC	A+BC
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

A	B	C	B+C	$A(B+C)$	AB	AC	AB+AC
0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	0	0	0	0
1	0	0	0	0	0	0	0
1	0	1	1	1	0	1	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

2) Write the Boolean expression equivalent to the following logic circuits. Do not simplify.

(a)  $F = (A'B' \oplus AB' \oplus (BC'))'$

$$b) \quad G = (A+C)'(B+C')$$

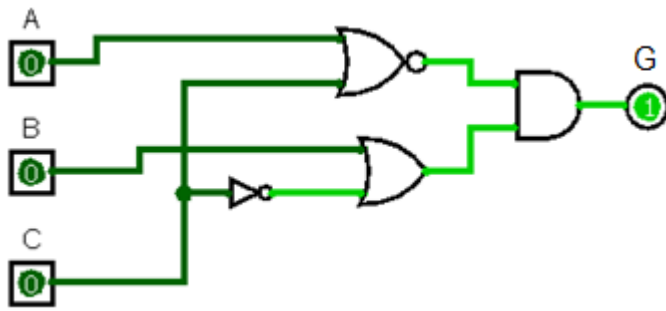

4) Using the following table:

- Obtain the logical expressions for **sum** and **Cout** (SOP).
- Obtain the simplified versions of **sum** and **Cout**.
- Draw the logic circuit for each function obtained in the part b.

A	B	Cin	sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**sum**      **B, Cin**

	00	01	11	10
<b>A</b> 0		1		1
1	1		1	

**Cout**      **B, Cin**

	00	01	11	10
<b>A</b> 0			1	
1		1	1	1

a)  $\text{sum} = A'.B'.\text{Cin} + A'.B.\text{Cin}' + A.B'.\text{Cin}' + A.B.\text{Cin}$

$\text{Cout} = A'.B.\text{Cin} + A.B'.\text{Cin} + A.B.\text{Cin}' + A.B.\text{Cin}$

b)

$\text{Cout} = B.\text{Cin} + A.\text{Cin} + A.B$


$\text{Sum} = A'.B'.\text{Cin} + A'.B.\text{Cin}' + A.B'.\text{Cin}' + A.B.\text{Cin}$

c)

	00	01	11	10
0			1	
1		1	1	1

	00	01	11	10
0			1	
1		1	1	1

	00	01	11	10
0			1	
1		1	1	1

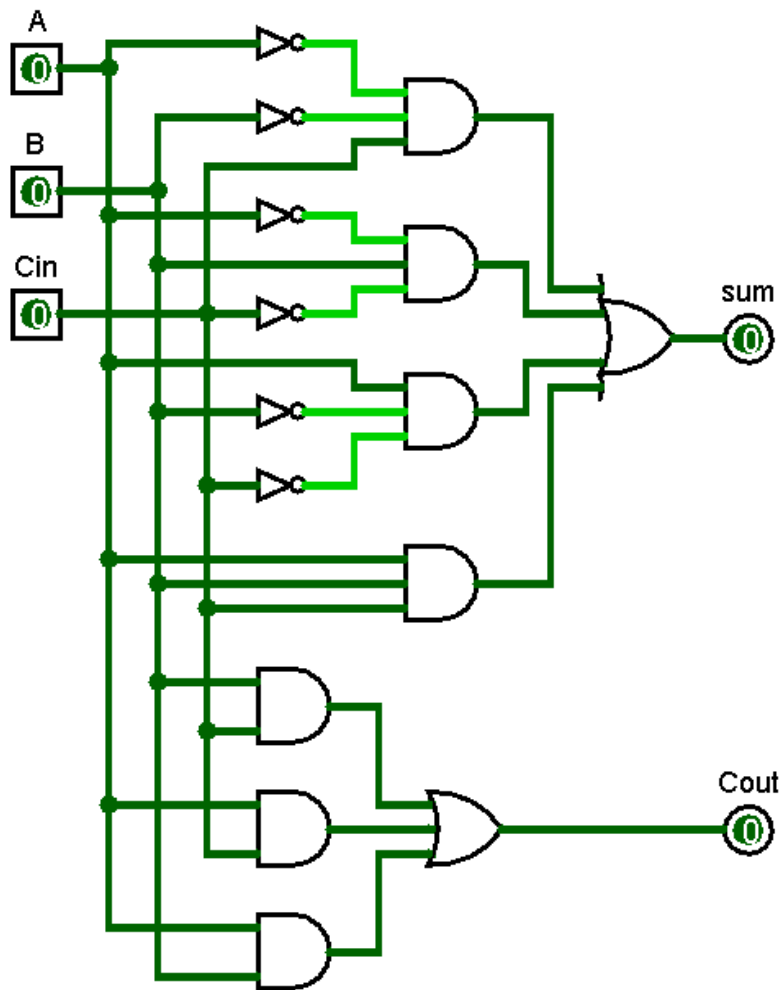

5) Simplify each of the following expressions.

$$\begin{aligned}
 \text{a) } & (A + B)(B + A') \\
 &= (A + B)B + (A + B)A' \\
 &= AB + BB + AA' + BA' \\
 &= AB + B + BA' \\
 &= AB + B(1 + A') \\
 &= AB + B \\
 &= (A + 1)B \\
 &= B
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } & A + B' + C + (AB')' \\
 &= A + B' + C + A + (B')' \\
 &= A + B' + C + A + B \\
 &= A + C + 1 \\
 &= 1
 \end{aligned}$$

$$\begin{aligned}
 \text{c) } & (B' + (AB)' + A + C)' \\
 &= (B' + A' + B' + A + C)' \\
 &= (B' + 1 + A + C)'
 \end{aligned}$$

$$= (1)'$$

$$= \emptyset$$