

Winter_25_Quiz_3 - Results



Attempt 1 of 1

Written Jan 28, 2025 7:57 PM - Jan 28, 2025 8:22 PM

Attempt Score **11.5 / 20 - 57.5 %**

Overall Grade (Highest Attempt) **11.5 / 20 - 57.5 %**

Question 1

Using the following table obtain F:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

☐ 1) $A'B'C + A'B'C' + AB'C' + AB'C$

✓ ☒ 2) $ABC' + ABC + A'BC + A'BC'$


☐ 3) $A'BC' + A'BC + AB'C' + ABC$

☐ 4)

$$A'B'C' + A'B'C + AB'C' + AB'C$$


Question 2

What is the value of $F = ?$

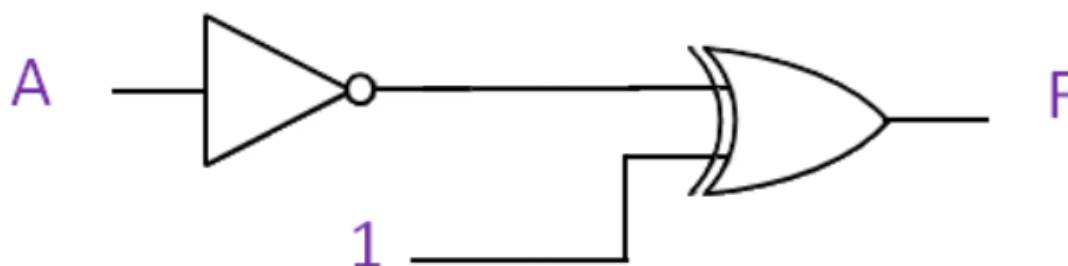☐ 0☒ 1☒ A ☐ A'

Question 3

Using the following circuit the value of F is :

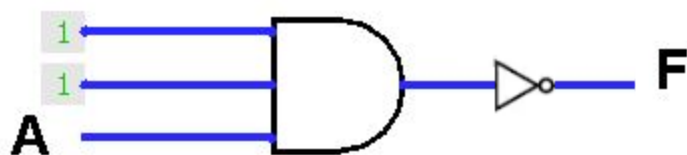☐ 1) A ☒ 2) A'

☐ 3) 1

☐ 4) 0

Question 4

If the number of Boolean variables is 3 then the number of Boolean functions can be built using these variables is equal to :

☐ 1) 512

☒ 2) 256

☐ 3) 8

☐ 4) 16

Question 5

Using Boolean identities, reduce the given Boolean expression:

$$F(X, Y, Z) = X'Y + YZ' + YZ + XY'Z'$$

$$X'Y + YZ' + YZ + XY'Z'$$

$$YZ' + YZ + X'Y + XY'Z'$$

$$Y(Z' + Z) + X'Y + XY'Z'$$

$$Y(1) + X'Y + XY'Z'$$

$$Y(1 + X') + XY'Z'$$

$$Y(1) + XY'Z'$$

$$Y + XY'Z'$$

The correct answer is not displayed for Written Response type questions.

▼ [Hide question 5 feedback](#)

Feedback

$$X'Y + YZ' + YZ + XY'Z'$$

$$Y(X' + Z' + Z) + XY'Z'$$


$$Y + XY'Z'$$

$$(Y+Y')(Y+XZ')$$

$$Y+XZ'$$

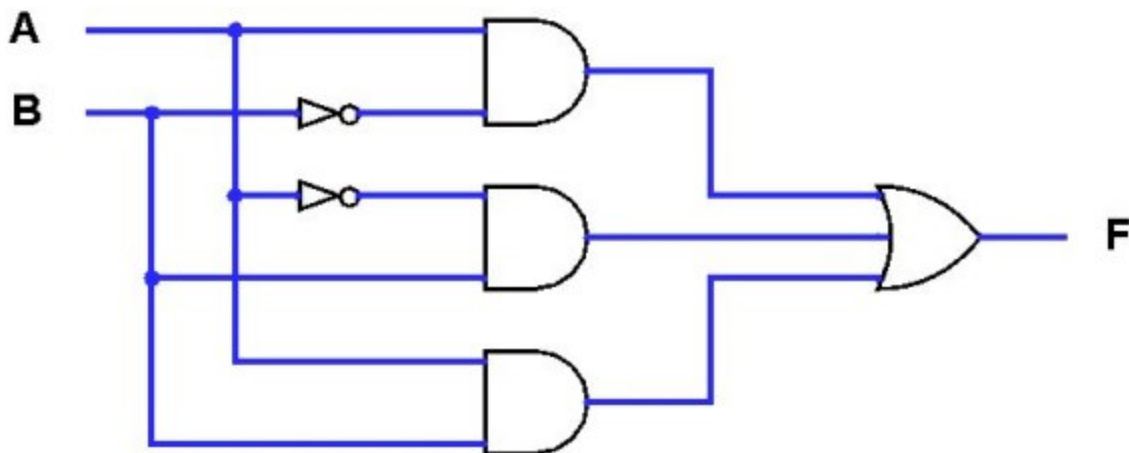Question 6

Considering the following circuit what is the value of F if A = 0 and B = 1



✓ ☒ 1) F = 1

☐ 2) F = 0

Question 7


There are ___8___ ✖ (16) Minterms for 4 variables (A, B, C, D)

Question 8

Write the Boolean expression equivalent to the following logic circuit:

+ (OR)

\oplus (XOR)

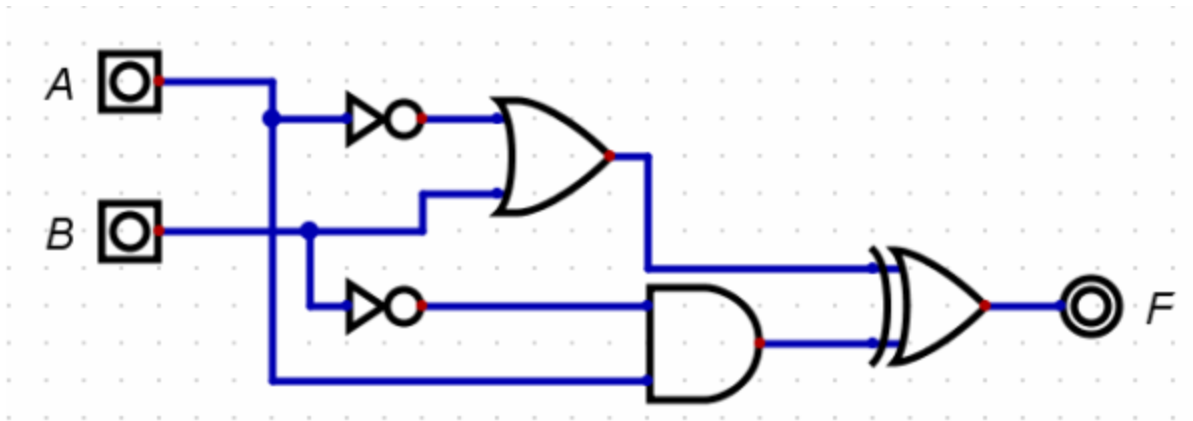

☒ 1) 1

☐ 2) $AB' + A' + B$

☐ 3) $A \oplus B$

Question 9

Simplify $F = A'B + AB' + B'$

☐ 1) $A + B'$

☒ 2) $A' + B'$

☐ 3) $A' + B$

☐ 4) $A + B$

Question 10

$$F = (A + A')' + AA'$$

After simplification, $F = ?$

✖ ☐ 1) 1

☐ 2) A'

☐ 3) A

➡ ☐ 4) 0

Done